Plant Monitor - wiring (Arduino Uno)

All sensors and modules powered from Uno 5V / GND. LEDs via 220 ohm resistors to GND. Matches wokwi/diagram.json.

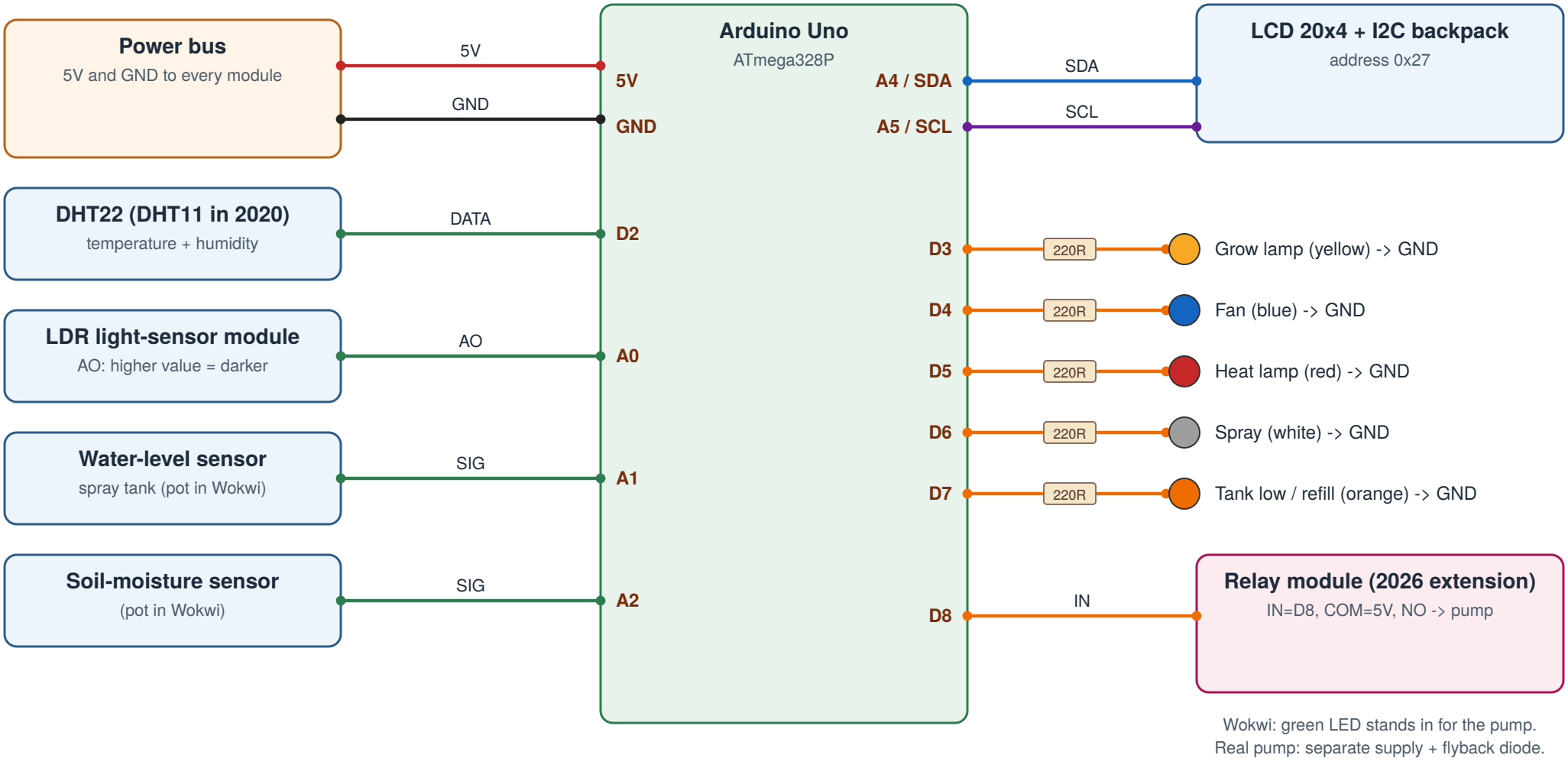

Wokwi: green LED stands in for the pump.
Real pump: separate supply + flyback diode.

2020 build: LEDs stood in for lamp, fan, heat lamp and spray. Pins 0/1 are left free for Serial (the 2020 sketch used them for LEDs).